

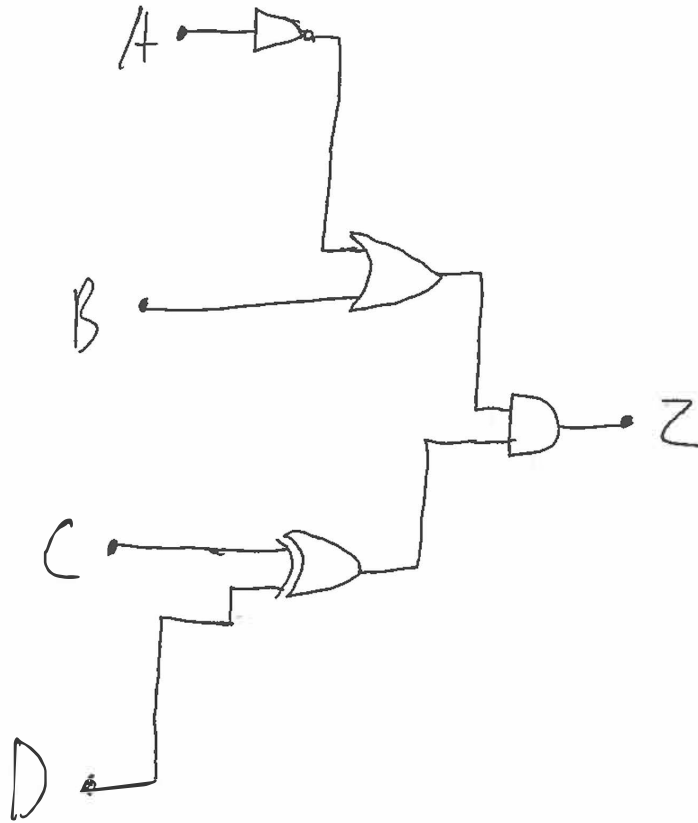


# Candidate 3 evidence


Task 1A

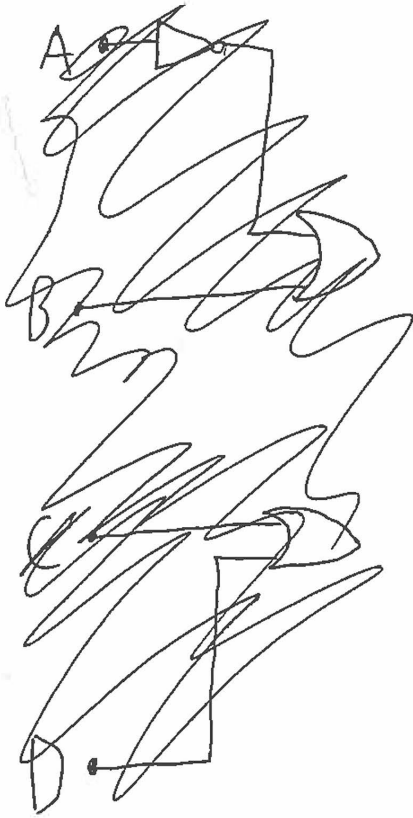

TASK 1B

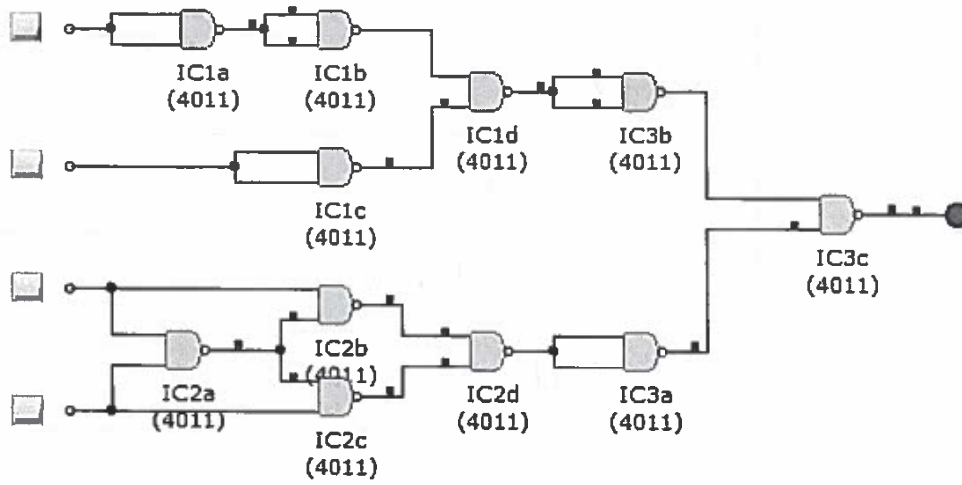

TASK 2A

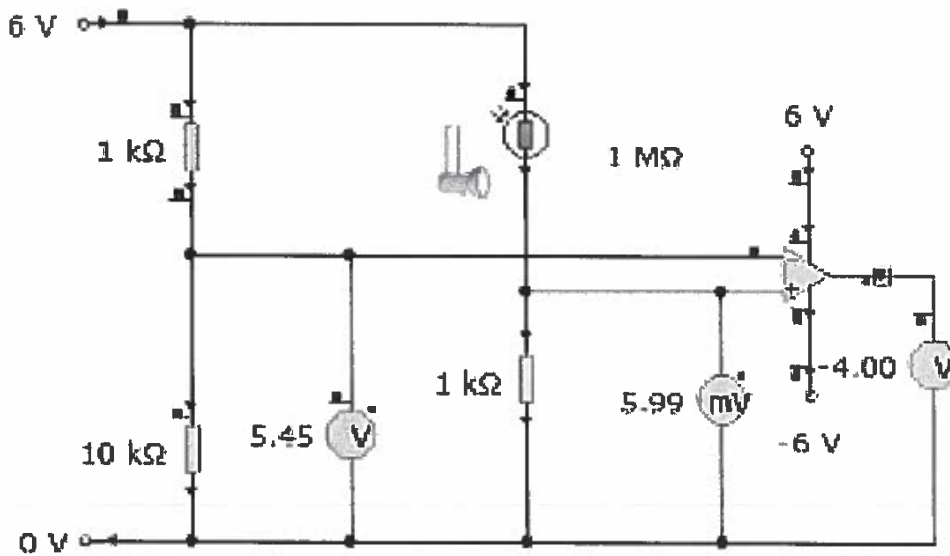

**Worksheet 1c**

Complete the actual results column on the truth table below.

A	B	C	D	Expected results	Actual results
0	0	0	0	0	
0	0	0	1	1	
0	0	1	0	1	
0	0	1	1	0	
0	1	0	0	0	
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	0	
1	0	0	0	0	0
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	0	0
1	1	0	0	0	
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	0	

(1 mark)

Task 1d

The results differ because the NAND equivalent circuit is wrong as there is an OR gate at the end where there should be an AND gate.

## Task 2E

When the ticket is scanned and dark is sensed the motor turns on on my circuit just like it should. However at first it didn't and I had to change the direction of the diode and change which part of the relay the motor is connected to. After removing the ticket when ~~darkness~~ darkness is ~~sensed~~ no longer sensed the motor will turn ~~off~~ slowly as its meant to. Before I amended the circuit the motor would turn on when the ticket was removed and light was sensed, this was fixed by switching the connection to the relay from the motor. The sensitivity can be changed by changing the resistance of the  $61k\Omega$  resistor.

Downloaded by

uk from

28/01/2019 13:58


**Worksheet 2d**

Complete the testing table shown below.


Planned test	Expected result	Actual result	Amendments made
Reduce the light level to minimum.	Motor turns.	Relay doesn't switch and motor doesn't turn	Switch the direction of the diode. Connect the motor to the other side of the <del>relay</del> relay. Return 6V rail connected to relay/diode and connect it to the rest of the circuit.
Alter the value of both the LDR and the fixed resistor to 6kΩ.	The motor turns on under different lighting conditions.	Motor switches on at any light level producing a resistance of more than 6kΩ	No amendments made.

(3 marks)

TASK 2C

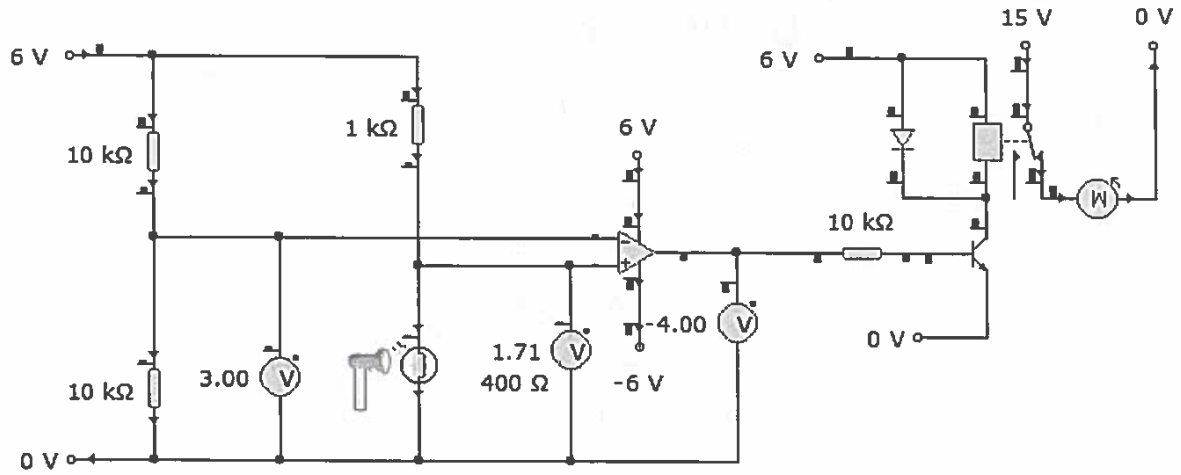

TASK 2E/2D

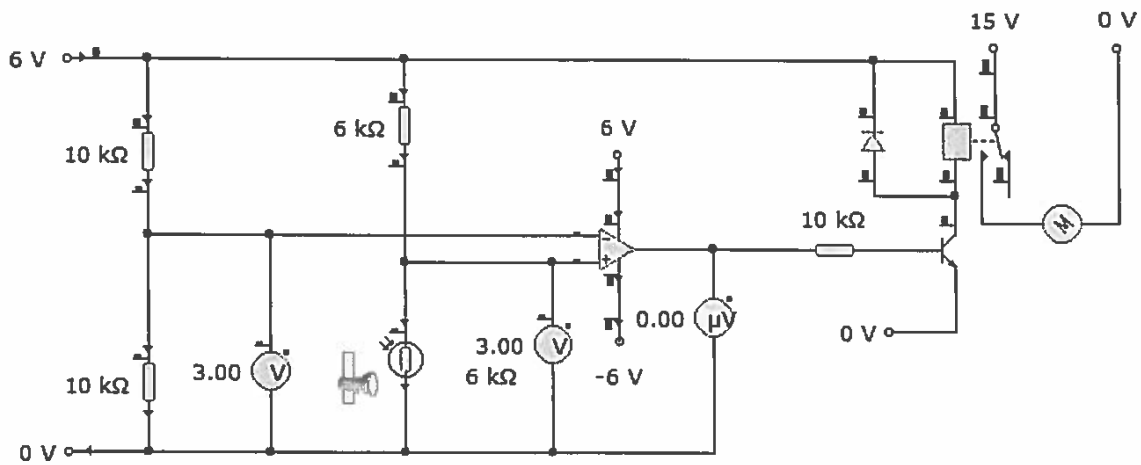

Downloaded by

uk from

on 28/01/2019 13:58

**Worksheet 2b**

Complete the testing table shown below.


Planned test	Expected result	Actual result	Amendments made
Reduce the light level to the minimum setting.	Op amp output saturates positive.	Op amp saturates negatively	Swap the position of the LDR and resistor.
Alter the light level until op amp changes state.	Op amp output changes state at 3V.	Op amp output changes state at 5.5V	Change the top 1k $\Omega$ resistor to 10k $\Omega$ .

(4 marks)

29



## TASK 3b

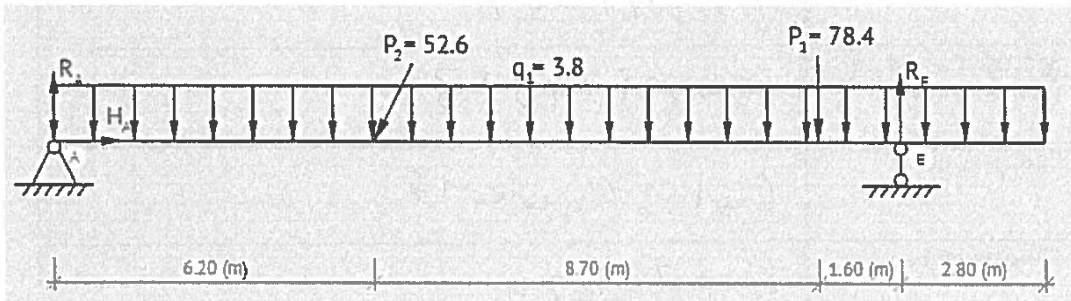

## Calculate the reactions at the supports of a beam

1. A beam is in equilibrium when it is stationary relative to an inertial reference frame. The following conditions are satisfied when a beam, acted upon by a system of forces and moments, is in equilibrium.

$$\sum F_x = 0: H_A - P_2 \cos(63) = 0$$

$\sum M_A = 0$ : The sum of the moments about the pin support at the point A:

$$-q_1 \cdot 19.3 \cdot (19.3/2) - P_2 \sin(63) \cdot 6.2 - P_1 \cdot 14.9 + R_E \cdot 16.5 = 0$$

$\sum M_E = 0$ : The sum of the moments about the roller support at the point B:

$$-R_A \cdot 16.5 + q_1 \cdot 19.3 \cdot (16.5 - 19.3/2) + P_2 \sin(63) \cdot 10.3 + P_1 \cdot 1.6 = 0$$

2. Calculate reaction of roller support at the point B:

$$R_E = (q_1 \cdot 19.3 \cdot (19.3/2) + P_2 \sin(63) \cdot 6.2 + P_1 \cdot 14.9) / 16.5 = (3.8 \cdot 19.3 \cdot (19.3/2) + 52.6 \cdot 0.891062 + 78.4 \cdot 14.9) / 16.5 = 131.30 \text{ (kN)}$$

3. Calculate reaction of pin support at the point A:

$$R_A = (q_1 \cdot 19.3 \cdot (16.5 - 19.3/2) + P_2 \sin(63) \cdot 10.3 + P_1 \cdot 1.6) / 16.5 = (3.8 \cdot 19.3 \cdot (16.5 - 19.3/2) + 52.6 \cdot \sin(63) \cdot 10.3 + 78.4 \cdot 1.6) / 16.5 = 67.31 \text{ (kN)}$$

4. Solve this system of equations:


$$H_A = P_2 \cos(63) = 52.60 \cdot 0.4540 = 23.88 \text{ (kN)}$$

5. The sum of the forces about the Gy axis is zero:


$$\sum F_y = 0: R_A - q_1 \cdot 19.3 - P_2 \sin(63) - P_1 + R_E = 67.31 \cdot 1 - 3.8 \cdot 19.3 - 52.6 \cdot 0.8910 - 78.4 + 131.30 \cdot 1 = 0$$

Vertical -  $R_A = 67.31 \text{ KN}$        $R_E = 131.3 \text{ KN}$   
 Horizontal -  $H_A = 23.88 \text{ KN}$       vertical



Table 3A

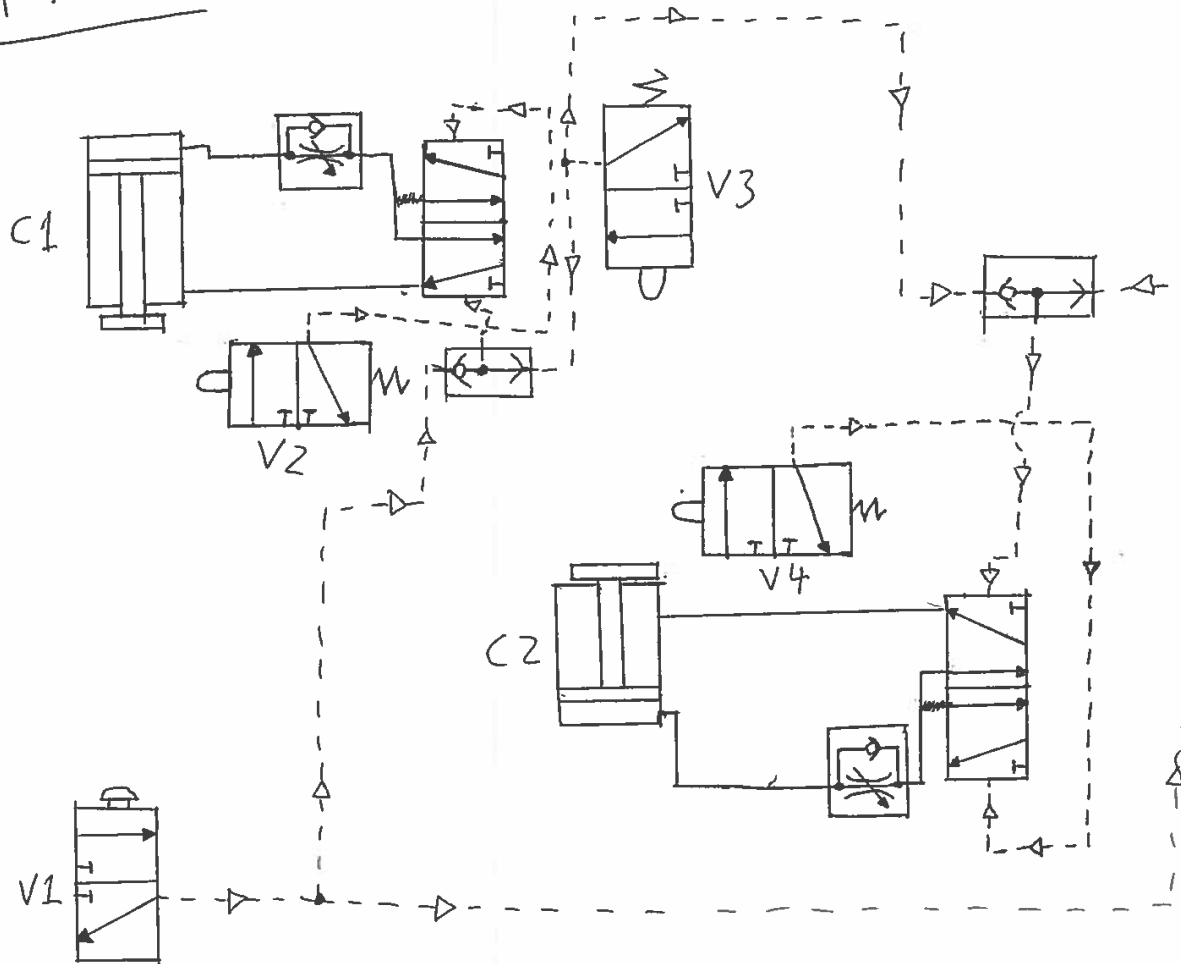

# Task 4

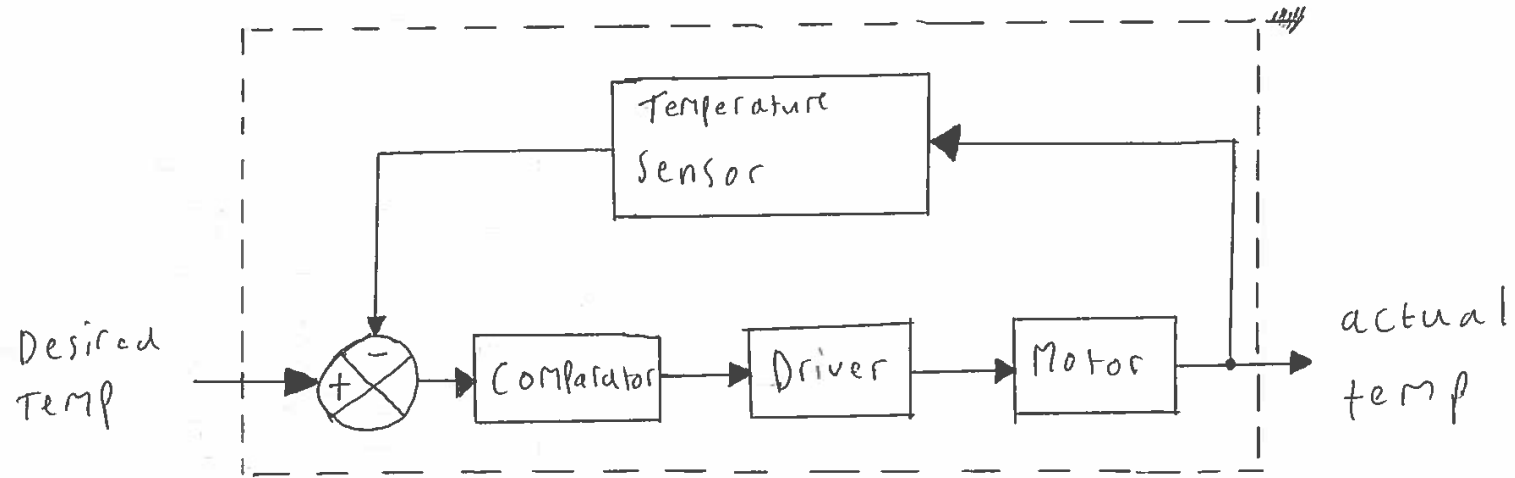

# TASK 5a

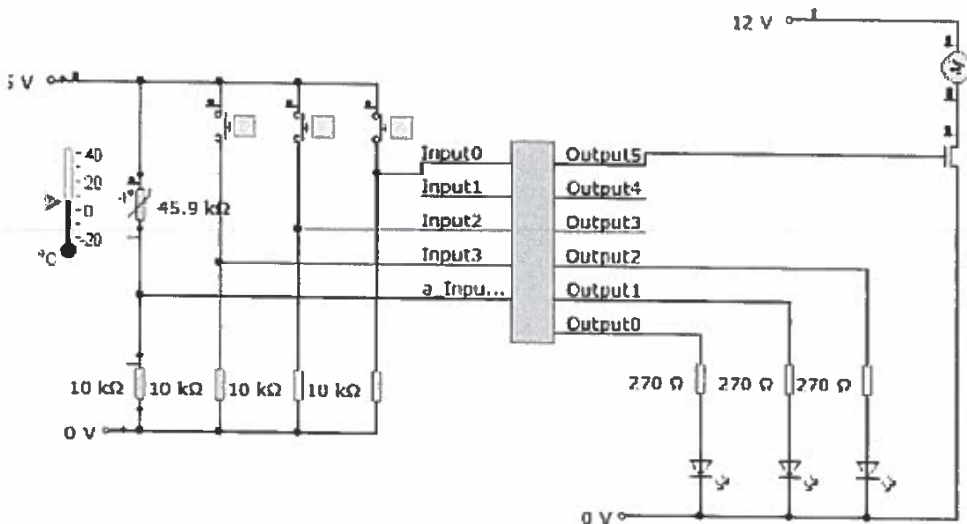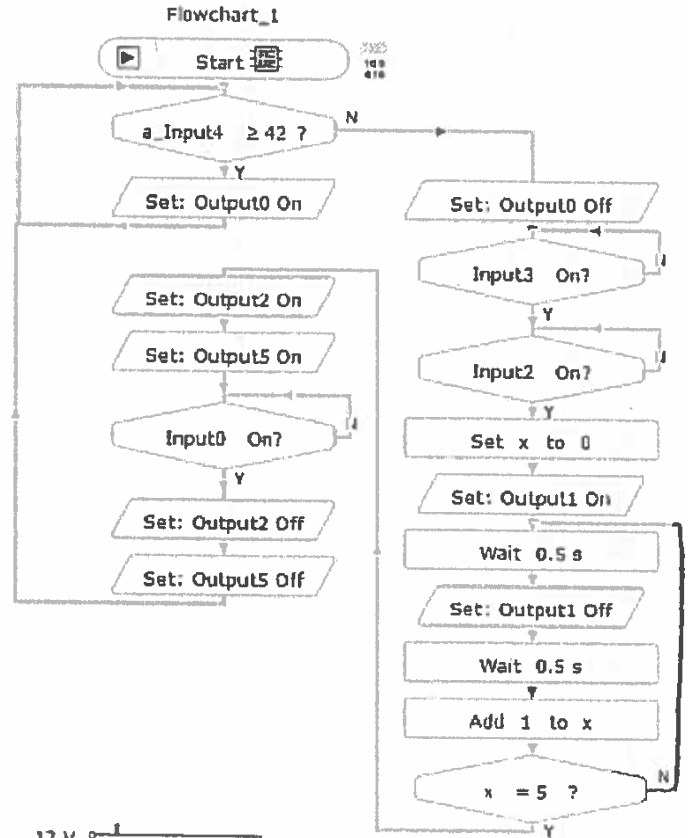

Downloaded by

on 28/01/2019 13:58

**Worksheet 5b**



Complete the testing table shown below.

Planned test	Expected result	Actual result	Amendments made
Adjust the thermistor temperature to its lowest value.	The 'temperature warning' indicator should be on.	The 'temperature warning' switches off and the flowchart <del>switch</del> moves onto next decision.	Changed sign in decision $a\_input4 \geq 42?$ to $a\_input4 \leq 42?$
Adjust the thermistor temperature to its highest value.	The 'temperature warning' indicator should switch off — the flowchart should progress to the next decision.	The 'temperature warning' switches off and the flowchart moves onto next decision.	No amendments made.
Press the 'harness safety check complete' switch and the 'operator switch' in sequence.	The 'harness safety check complete' indicator should flash five times.	The 'harness safety check <del>complete</del> indicator doesn't flash five times	Move the arrow from decision <del>xxx</del> $x=5?$ from after set:output1 on to before set:output1 off

(5 marks)

33

# TASK 5c

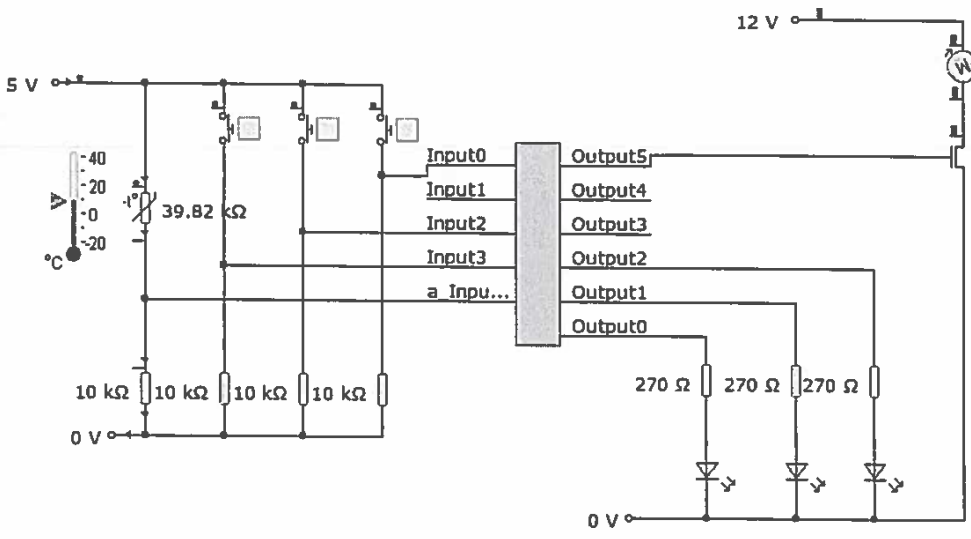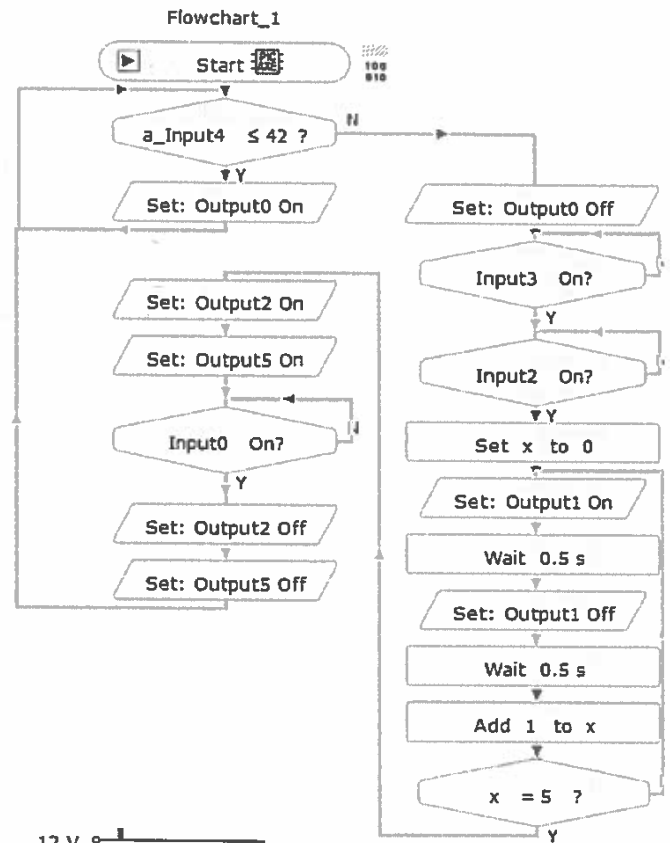

## Task 5d

My solution meets specification point I as when the temperature drops below a set value a warning indicator switches on. Specification point II is also met as it requires a safe temperature and both switches to be pulled in order to work. The third specification point is also met as after passing the 'harness safety check complete switch' the indicator will flash 5 times. Finally specification point IV is also met as the motor and 'ride on' indicator stay on until the ride ends. Overall my solution is very effective in controlling the safety checks as it makes sure each one is done before continuing as well as using indicators to tell people what is happening.