

Candidate 2 evidence (Batteries)

Batteries

Aim
I am going to measure the internal resistance of a 1.5V battery using two methods

Underlying Physics

An electrical cell is made from materials (metal or chemicals for example). All materials have some resistance. Therefore a cell must have resistance. This resistance is called the INTERNAL RESISTANCE of the cell. (1)

You can think of a battery as a source of voltage (emf) and a resistance, like this diagram.

If you connect the battery into a circuit with another resistor R , a current will flow through the circuit and there will be a voltage across R and the same voltage across the battery. This is called V , the terminal potential difference (t.p.d.)

V is less than E because of the resistance of the battery inside. (r)


Using Ohm's Law,
 $E = I(R+r)$ and $V = IR$
 so $V = E - Ir$
 and a graph of V against I will have a gradient of $-r$.

also $V = IR$
 so $V = I / \frac{1}{R}$

And a graph of R against V will hit the R axis at π .

Method

I set up this circuit

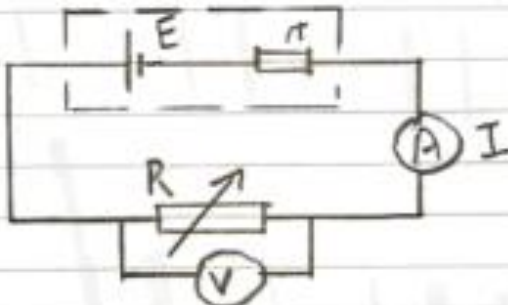

I was measured using a digital multimeter on the Amps setting.

V was measured using a digital multimeter on the Volts setting.

R was a resistance box.

Table

Voltmeter reading (V)	Ammeter reading (A)
1.32	0.35
1.24	0.44
1.16	0.64
1.08	0.78
0.94	0.91
0.77	1.43


The scale reading uncertainty in the ammeter was ± 0.01 A and in the voltmeter was ± 0.01 V

Graph


The graph of Voltage V is on the next page

The gradient of the graph is 0.555, and so the internal resistance of the battery is

0.555 Ω .

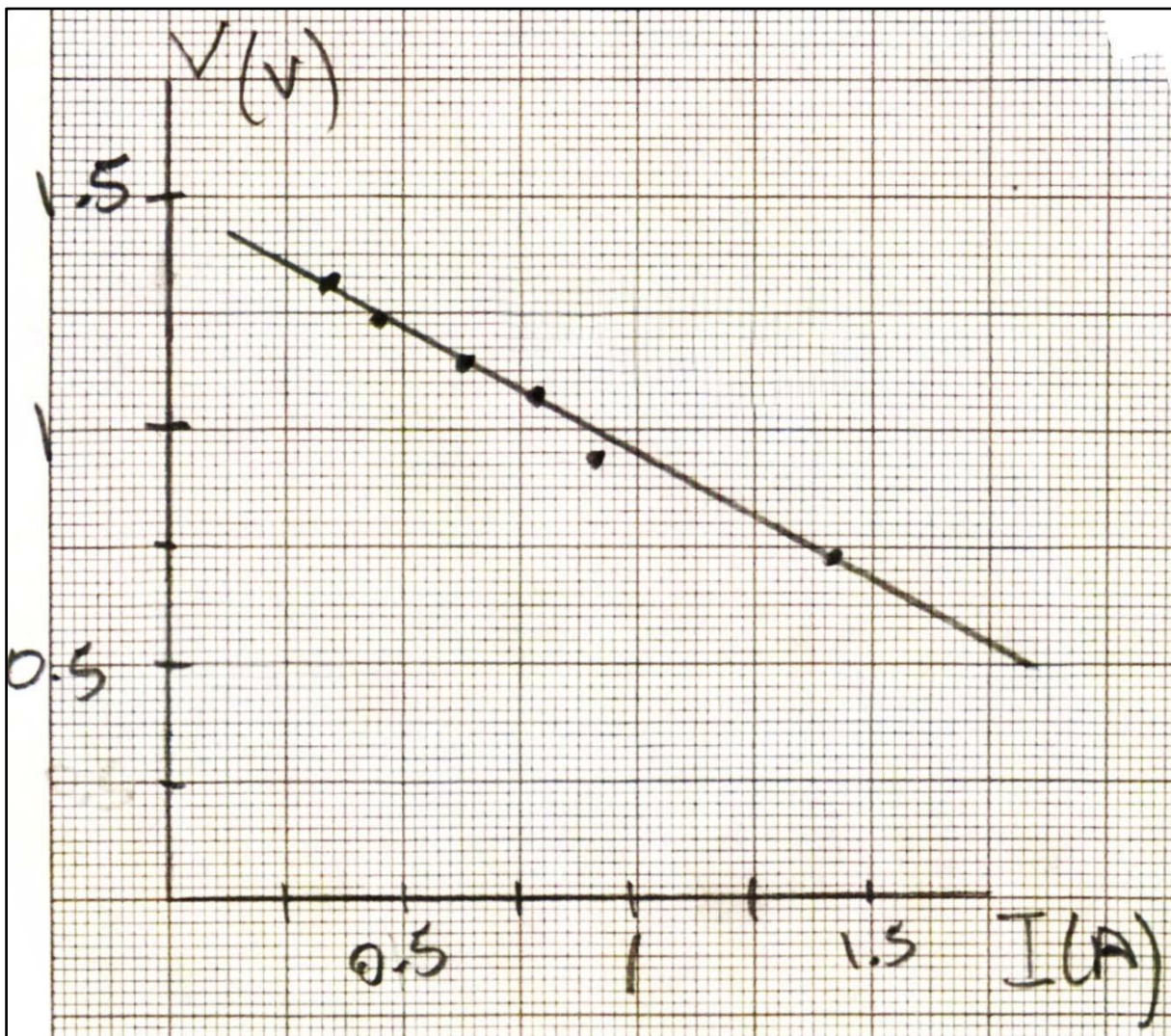

I set up this circuit

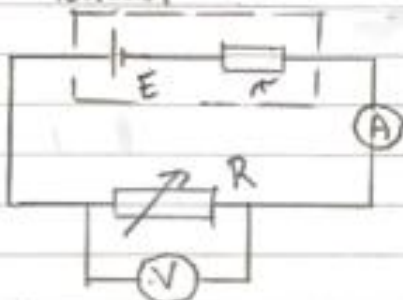

I was measuring using a digital multimeter on the Amps setting

R was measured using a digital multimeter on the Ohms setting.

R was a resistance box.

Table


<u>Ohmmeter Reading (V)</u>	<u>Ammeter reading (A)</u>	<u>$1/I$ (A⁻¹)</u>
0.53	1.75	0.57
1.61	0.76	1.32
2.33	0.55	1.82
3.22	0.41	2.44
4.27	0.32	3.13
5.19	0.27	3.70

The scale reading uncertainty in the ammeter was ± 0.01 A and in the Ohmmeter was $\pm 0.01 \Omega$

Graph

The graph of R against $1/I$ is on the next page

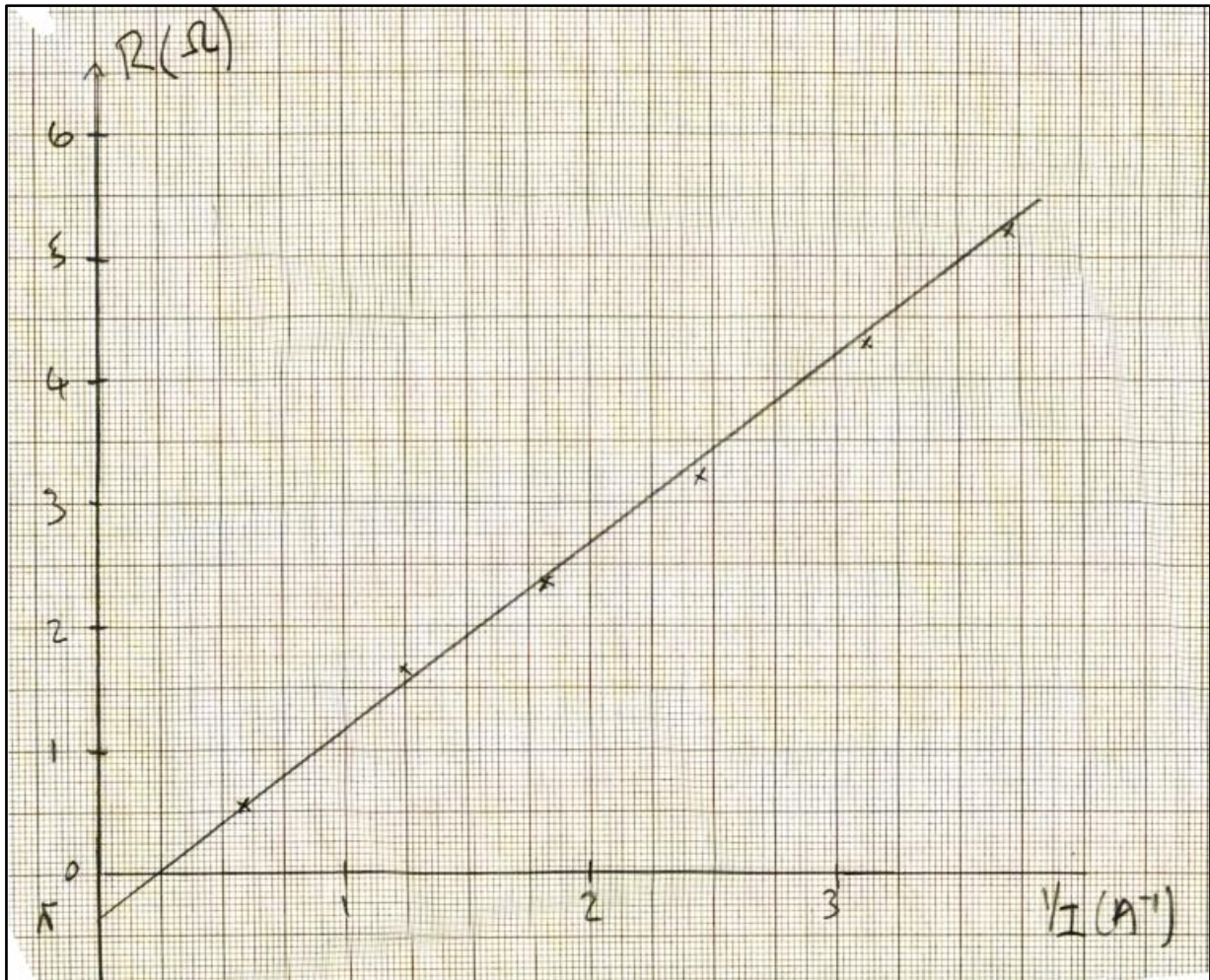The intercept on the y-axis is 0.45, so the internal resistance is 0.45 Ω .



Conclusion

The first experiment gave me $r = 0.555 \Omega$ and the second was $r = 0.45 \Omega$, so my average internal resistance is

$$(0.555 + 0.45) \div 2 = 0.5025 \Omega$$

Evaluation

The multimeters only read to 2 decimal places. If I had meters that read to more decimal places, the readings would have been more accurate.

I could have repeated my measurements and worked out a random uncertainty. This would have made the errors in my results more realistic, because the reading uncertainty in the metres was very small.

I could have tried to find the internal resistance of another 1.5V battery to compare with the one I used to see if my results were correct.

Reference

1. <https://www.bbc.co.uk/education/guides/zxx665g/revision>.